

# Digital Circuits and Systems - Verilog

## ECS 326/676

**Course Instructor:** Dr. Santanu Talukder

**Teaching Assistant:** Ishanya  
[ishanya21@iiserb.ac.in](mailto:ishanya21@iiserb.ac.in)

**Department:** Electrical Engineering and Computer Science  
Indian Institute of Science Education and Research, Bhopal

Jan 2025 – Apr 2025



# Introduction

## What is Digital Design?

- ▶ Design of circuits that process digital signals (0s and 1s).
- ▶ Used in computing, communication, and embedded systems.
- ▶ Everything in Digital Circuits and Systems-ECS 326/676, so pay attention in class xD

## Why Hardware Description Languages (HDLs)?

- ▶ Manual circuit design is complex and error-prone.
- ▶ HDLs describe hardware behavior at an abstract level.
- ▶ Used for simulation, synthesis, and FPGA/ASIC design.

## Verilog vs. Programming Languages

- ▶ **C:** Executes sequentially on a CPU.
- ▶ **Verilog:** Describes hardware that works in parallel.



# Introduction to Verilog

## What is Verilog?

- ▶ A **Hardware Description Language (HDL)** used to model digital circuits.
- ▶ Describes circuit behavior, structure, and timing.
- ▶ Used for designing and simulating hardware before fabrication.

## Where is Verilog Used?

- ▶ **FPGA (Field-Programmable Gate Arrays):** Reconfigurable hardware.
- ▶ **ASIC (Application-Specific Integrated Circuits):** Custom-designed chips.
- ▶ **VLSI (Very Large-Scale Integration):** High-density integrated circuits.



# What should you know?

- ▶ Combinational vs. Sequential Circuits
- ▶ Logic Gates: AND, OR, NOT, XOR
- ▶ Truth tables
- ▶ FSMs
  - ▶ Model systems with defined states and transitions.
  - ▶ Types: **Moore** (output depends only on state) and **Mealy** (output depends on state + input).
  - ▶ Used in control logic, counters, and protocol design.



# Verilog Design Flow with Icarus Verilog

1. **Write Verilog Code:** Define circuit behavior.
2. **Compile with Icarus Verilog:** Use iverilog to generate an executable.
3. **Simulate with VVP:** Run the compiled output using vvp.
4. **View Waveforms in GTKWave:** Generate waveform output (.vcd) for debugging. Analyze results visually.



# Testbench

- ▶ A **testbench** is a separate module used to verify circuit behavior.
- ▶ It applies **stimulus** (inputs) and observes the outputs.
- ▶ Common commands:
  - ▶ `$monitor` – Displays signal values during simulation.
  - ▶ `$display` – Prints custom messages in the simulation output.
  - ▶ `#delay` – Introduces time delays in testbenches.



# Basic Syntax in Verilog

- ▶ Module Definition: Every Verilog design starts with a 'module' declaration.
- ▶ End Statement: Use 'endmodule' to indicate the end of a module.
- ▶ Do not start names with numbers.
- ▶ White spaces are ignored.
- ▶ Comments:
  - ▶ // for single-line comments.
  - ▶ /\* ... \*/ for multi-line comments.
- ▶ Case Sensitivity: Verilog is case-sensitive (module is not the same as MODULE).
- ▶ Semicolon (;): Required at the end of each statement.



# Verilog Data Types

- ▶ **wire** - Represents combinational logic.
- ▶ **reg** - Stores values, used in sequential logic.
- ▶ **integer** - Stores whole numbers.
- ▶ **parameter** - Defines constants.

```
wire A, B;  
reg C;  
integer count;  
parameter WIDTH = 8;
```





# Operators in Verilog (1/3): Arithmetic, Logical, Relational

- ▶ **Arithmetic Operators:**

- ▶ +, -, \*, /, %

- ▶ **Logical Operators:**

- ▶ &&, ||, !

- ▶ **Relational Operators:**

- ▶ >, <, >=, <=, ==, ==

```
assign sum    = a + b;  
assign flag   = (a > b) && (c != d);  
assign eq     = (a == b);
```



# Operators in Verilog (2/3): Bitwise and Shift

- ▶ **Bitwise Operators:**

- ▶ `&`, `|`, `^`, `~`

- ▶ **Shift Operators:**

- ▶ `<<` (left shift) and `>>` (right shift)

```
assign bit_and = a & b;  
assign shifted = a << 2;
```



# Operators in Verilog (3/3): Concatenation & Replication

## ► Concatenation:

- Uses braces {...}
- Combines multiple bits or buses.

## ► Replication:

- Uses braces with a repetition factor {N{expr}}

```
assign combined    = {a[2], a[1], a[0]};  
assign replicated  = {4{a[0]}};
```



# HDL Implementation: Structural (Gate-Level)

- ▶ Defines design by interconnecting basic gates and modules.
- ▶ Uses explicit instantiation of lower-level primitives.
- ▶ Offers detailed representation at the transistor or gate level.

```
module random_xor(input a, b, output y);  
    xor g1 (a, b, y)  
endmodule
```



# HDL Implementation: Behavioral

- ▶ Describes functionality using high-level constructs.
- ▶ Uses procedural blocks such as `always` and `initial`.
- ▶ Abstracts the detailed gate-level connections.

```
module and_gate(input a, input b, output y);  
    assign y = a & b;  
endmodule
```



# Initial vs. Always in Verilog

**Initial:** Process executes exactly once.

```
initial begin
    a = 1;
    #1;
    b = a;
end
```

**Always:** Process is rescheduled many times.

```
always @(a or b)
begin
    if (a)
        c = b;
    else
        d = ~b;
end
```



# Procedural Assignment in Verilog

- ▶ **Blocking Assignment ( = )**
  - ▶ Executes statements sequentially.
  - ▶ Used for combinational logic.
  - ▶ Statement order is strictly followed.
- ▶ **Non-Blocking Assignment ( <= )**
  - ▶ Statements are scheduled concurrently.
  - ▶ Common in sequential (clocked) logic.
  - ▶ Allows switching values without temporary storage.



# Blocking vs. Non-Blocking Example

## Blocking Assignment Example:

```
initial begin
    a = 1;    // executes immediately
    b = a;    // b gets the updated value of a
end
```

## Non-Blocking Assignment Example:

```
always @(posedge clk) begin
    a <= b;    // scheduled concurrently
    b <= a;    // old value of a is used
end
```





# AND and OR Gate Modules

Is this structural or behavioral implementation ?

```
// 3-input AND gate module  
module and3 (output Y, input A, B, C);  
    and (Y, A, B, C);  
endmodule
```

```
// 3-input OR gate module  
module or3 (output Y, input A, B, C);  
    or (Y, A, B, C);  
endmodule
```



## Testbench for AND and OR Gates (1/2)

```
// Testbench to test both AND and OR gates
module tb_gate;
    reg A, B, C;
    wire Y_and, Y_or;

    // Instantiate the 3-input AND gate
    and3 u1 (.Y(Y_and), .A(A), .B(B), .C(C));

    // Instantiate the 3-input OR gate
    or3 u2 (.Y(Y_or), .A(A), .B(B), .C(C));
```



## Testbench for AND and OR Gates (2/2)

```
initial begin
    // Monitor changes in signals
    $monitor("Time: %0d | A=%b B=%b C=%b |
              AND Output=%b OR Output=%b",
              $time, A, B, C, Y_and, Y_or);
    A = 0; B = 0; C = 0; #10;
    A = 0; B = 0; C = 1; #10;
    A = 0; B = 1; C = 0; #10;
    A = 0; B = 1; C = 1; #10;
    A = 1; B = 0; C = 0; #10;
    A = 1; B = 0; C = 1; #10;
    A = 1; B = 1; C = 0; #10;
    A = 1; B = 1; C = 1; #10;
    $finish;
end
endmodule
```



# Run in Terminal

```
C:\iverilog\bin>iverilog -o gate_test gate_test.v
```

```
C:\iverilog\bin>vvp gate_test
```


Time: 0		A=0	B=0	C=0		AND Output=0	OR Output=0
Time: 10		A=0	B=0	C=1		AND Output=0	OR Output=1
Time: 20		A=0	B=1	C=0		AND Output=0	OR Output=1
Time: 30		A=0	B=1	C=1		AND Output=0	OR Output=1
Time: 40		A=1	B=0	C=0		AND Output=0	OR Output=1
Time: 50		A=1	B=0	C=1		AND Output=0	OR Output=1
Time: 60		A=1	B=1	C=0		AND Output=0	OR Output=1
Time: 70		A=1	B=1	C=1		AND Output=1	OR Output=1



# GTKWave

## Terminal Command

`gtkwave gate_test.vcd`

 

# Half Adder Module (Structural)

```
module HA(input x, y, output b, d);  
    // Generate carry: AND gate  
    and g2(b, x, y);    // b = x AND y  
  
    // Generate sum (difference): XOR gate  
    xor g3(d, x, y);    // d = x XOR y  
endmodule
```



# Full Subtractor

```
module fs(input a, b, c, output bo, d);
  wire na;
  wire x, y, z;

  not g0(na, a);
  xor g1(d, a, b, c);
  or g2(x, c, b); //borrow
  and g3(y, na, x);
  and g4(z, c, b);
  or g5(bo, y, z);
endmodule

module tb_fs;
  reg a, b, c;
  wire bo, d;
  fs uut (.a(a), .b(b), .c(c), .d(d), .bo(bo));

  initial begin
    $dumpfile("fs.vcd");
    $dumpvars(0, tb_fs);
    $monitor("Time %t, a = %b, b = %b, c = %b, bo = %b, d = %b", $time, a, b, c, bo, d);

    #1; a = 0; b = 0; c = 0;
    #10; a = 0; b = 0; c = 1;
    #1; a = 0; b = 1; c = 0;
    #1; a = 0; b = 1; c = 1;
    #1; a = 1; b = 0; c = 0;
    $finish;
  end
endmodule
```



# Random Function

```
module fun(input a, b, c, output y);  
  
    assign y = a & ~b | ~b & ~c | ~a & b & c;  
  
endmodule  
  
module tb_fun;  
    reg a, b, c;  
    wire y;  
    fun uut (.a(a), .b(b), .c(c), .y(y));  
  
    initial begin  
        $dumpfile("func.vcd");  
        $dumpvars(0, tb_fun);  
  
        $monitor(" Time %t, a = %b, b = %b, c = %b, y = %b", $time, a, b, c, y);  
  
        #10; a = 0; b = 0; c = 0;  
        #10; a = 0; b = 0; c = 1;  
        #10; a = 0; b = 1; c = 0;  
        #10; a = 1; b = 0; c = 1;  
        #10; a = 1; b = 0; c = 1;  
        #10; a = 1; b = 1; c = 0;  
        #10; a = 1; b = 1; c = 1;  
        #10; a = 1; b = 1; c = 1;  
  
        $finish;  
    end  
  
endmodule
```





## 3 to 8 Decoder

```
module decoder3to8(input a2, a1, a0, output y0, y1, y2, y3, y4, y5, y6, y7);  
    wire na2, na1, na0;  
  
    // Invert the inputs to create not versions of a2, a1, a0  
    not n0(na2, a2); // na2 = NOT a2  
    not n1(na1, a1); // na1 = NOT a1  
    not n2(na0, a0); // na0 = NOT a0  
  
    // Create AND gates for each output  
    and g0(y0, na2, na1, na0); // 000  
    and g1(y1, na2, na1, a0); // 001  
    and g2(y2, na2, a1, na0); // 010  
    and g3(y3, na2, a1, a0); // 011  
    and g4(y4, a2, na1, na0); // 100  
    and g5(y5, a2, na1, a0); // 101  
    and g6(y6, a2, a1, na0); // 110  
    and g7(y7, a2, a1, a0); // 111  
endmodule
```



## 3 to 8 Decoder Testbench

```
module tb_decoder3to8;
    reg a2, a1, a0;
    wire y0, y1, y2, y3, y4, y5, y6, y7;

    // Instantiate the 3-to-8 decoder
    decoder3to8 uut (.a2(a2), .a1(a1), .a0(a0),
                   .y0(y0), .y1(y1), .y2(y2), .y3(y3),
                   .y4(y4), .y5(y5), .y6(y6), .y7(y7));

    initial begin
        // Create the VCD file for waveform analysis
        $dumpfile("decoder3to8.vcd");
        $dumpvars(0, tb_decoder3to8);

        // Display the results in the console
        $monitor("Time %t, a2 = %b, a1 = %b, a0 = %b, y0 = %b, y1 = %b, y2 = %b,
                y3 = %b, y4 = %b, y5 = %b, y6 = %b, y7 = %b",
                $time, a2, a1, a0, y0, y1, y2, y3, y4, y5, y6, y7);

        // Apply test cases for the decoder inputs
        #10 a2 = 0; a1 = 0; a0 = 0; // Select y0
        #10 a2 = 0; a1 = 0; a0 = 1; // Select y1
        #10 a2 = 0; a1 = 1; a0 = 0; // Select y2
        #10 a2 = 0; a1 = 1; a0 = 1; // Select y3
        #10 a2 = 1; a1 = 0; a0 = 0; // Select y4
        #10 a2 = 1; a1 = 0; a0 = 1; // Select y5
        #10 a2 = 1; a1 = 1; a0 = 0; // Select y6
        #10 a2 = 1; a1 = 1; a0 = 1; // Select y7

        // Finish the simulation
        $finish;
    end
endmodule
```



## 4 to 2 Encoder

```
module en4to2(input [3:0] in , output reg [1:0] out);  
    always @(*) begin  
        case (in)  
            4'b0001: out = 2'b00; // Input: 0001 → Output: 00  
            4'b0010: out = 2'b01; // Input: 0010 → Output: 01  
            4'b0100: out = 2'b10; // Input: 0100 → Output: 10  
            4'b1000: out = 2'b11; // Input: 1000 → Output: 11  
            default: out = 2'b00; // Default: Catch invalid inputs  
        endcase  
    end  
endmodule
```



## 4 to 2 Encoder Testbench

```
module tb_en4to2;
    reg [3:0] in;           // Input to test the encoder
    wire [1:0] out;         // Output from the encoder

    // Instantiate the 4-to-2 Encoder
    en4to2 uut (
        .in(in),
        .out(out)
    );

    // Testbench logic
    initial begin
        // Initialize GTKWave dump
        $dumpfile("en4to2.vcd");
        $dumpvars(0, tb_en4to2);

        // Display signal values on console
        $monitor("Time: %0t | Input: %b | Output: %b", $time, in, out);

        // Test cases
        in = 4'b0000; #10; // Invalid input
        in = 4'b0001; #10; // Expected Output: 00
        in = 4'b0010; #10; // Expected Output: 01
        in = 4'b0100; #10; // Expected Output: 10
        in = 4'b1000; #10; // Expected Output: 11
        in = 4'b1010; #10; // Invalid input

        // End simulation
        $finish;
    end
endmodule
```



## 8 to 3 Priority Encoder

```
module pe(input [7:0] in , output reg [2:0] out);
always @(*)
begin
if (in[7]) out = 3'b111;
else if (in[6]) out = 3'b110;
else if (in[5]) out = 3'b101;
else if (in[4]) out = 3'b100;
else if (in[3]) out = 3'b011;
else if (in[2]) out = 3'b010;
else if (in[1]) out = 3'b001;
else if (in[0]) out = 3'b000;
else out = 3'b000;
end
endmodule

module tb_pe; //Testbench
reg [7:0] in;
wire [2:0] out;
pe uut(.in(in), .out(out));
initial begin

$dumpfile("pe.vcd");
$dumpvars(0, tb_pe);
$monitor("Time %t, in = %b, out = %b", $time, in, out);
#10; in = 8'b0000_0010;
#10; in = 8'b0000_0001;
#10; in = 8'b0000_0100;
#10; in = 8'b0000_1000;
#10; in = 8'b0010_0000;
#10; in = 8'b0100_0000;
$finish;
end
endmodule
```



# Practice Questions: Verilog Coding

Try both structural and behavioral implementation. You are free to combine both too.

1. Write a Verilog module for a 2-to-1 Multiplexer.
2. Write a Verilog module for a 1-to-4 Demultiplexer.
3. Write a Verilog module for a positive edge-triggered D Flip-Flop.
4. Write a Verilog module for a 4-bit Binary Counter.
5. Write a Verilog module for a Half Adder, Full Adder, Half subtractor, Full subtractor.



# References

- ▶ **Course:** ECS 326/676 2023-24 by Dr. Santanu Talukder.
- ▶ **Course:** ECS409/609 Computer Organisation 2024-25
- ▶ **Textbook:** Digital design by Morris Mano (5th edition)
- ▶ **Textbook:** *Digital Design and Computer Architecture*, Chapter 4, by Sarah Harris and David Harris.
- ▶ **GitHub Repository:**  
[https://github.com/ishanyaa/computer\\_organisation](https://github.com/ishanyaa/computer_organisation)
- ▶ Youtube and Internet. (Our Lord and Saviour xD)

PS: Let me know, if there are any mistakes and I will update the slides.



# Advice

## A Word of Advice:

Should you encounter difficulties or find yourself stuck, remember that help is always within reach. Whether it be asking for guidance from your profs/peers or exploring the wealth of resources available on the internet, do not hesitate to seek assistance. Embrace challenges as opportunities for growth, for as the adage goes, *"Practice makes you perfect; Every line of code brings you closer to mastery."* Push the boundaries of your knowledge! Happy learning Verilog :)



Source: Internet

