

# Indian Institute of Science Education and Research, Bhopal

## ECS 326/676: Digital Circuits and Systems

Ishanya, Department of EECS

January-April ,2025

### Instructions

Kindly let me know if there are any updates or corrections that need to be made. Good luck and have fun!

For any queries/clarifications/mistakes, feel free to reach out to me at [ishanya21@iiserb.ac.in](mailto:ishanya21@iiserb.ac.in).

**Note:** You can try out more questions beyond the ones listed here. This is not the end of it. All decisions are up to the instructor of the course.

### Questions

#### 1. Boolean Algebra

1. Simplify the following Boolean expression:  $A \cdot (B + C) + A' \cdot (B' + C')$ .
2. Using Boolean algebra, prove that  $A + AB = A$ .
3. Simplify the expression  $(A' + B' + C)(A + B + C)(A' + B)$  using Boolean algebra.
4. Prove that  $(A \cdot B) + A' = (A + B) \cdot (A' + B')$  using Boolean identities.
5. Derive a minimal SOP (Sum of Products) form for the Boolean function  $F(A, B, C, D) = A'BC + AB'C + A'B'C'$ .

#### 2. Simplify the Function

1. Simplify the function  $F(A, B, C) = AB + A'C + B'C$  using Boolean algebra.
2. Given the Boolean function  $F(A, B, C, D) = AB + A'C + B'D$ , find its minimal representation using Boolean identities and Karnaugh maps.
3. Find the simplest expression for  $F(A, B, C, D) = A'BC + AB'C' + AC$  using Boolean algebra and Karnaugh maps.
4. Using Boolean algebra, simplify  $F(A, B, C, D, E) = AB + A'C + BC'D$ , and implement it with the minimum number of gates.
5. Derive the minimal Boolean expression for the function  $F(A, B, C) = A'B + A'BC + A'B'C$ .

#### 3. Number Systems: Binary, Decimal, Octal, Hexadecimal

1. Convert the binary number  $1011011_2$  to its equivalent decimal, octal, and hexadecimal forms.
2. Perform the subtraction  $110101_2 - 10101_2$  and express the result in hexadecimal.
3. Convert the octal number  $345_8$  to binary, decimal, and hexadecimal.
4. Convert the hexadecimal number  $C7_{16}$  to binary, octal, and decimal.
5. Perform the addition of  $101110_2$  and  $110111_2$  and express the result in both binary and hexadecimal.

#### 4. Complement of a Function

1. Find the complement of the Boolean function  $F = (A + B)(C + D)(A' + B')$ .
2. Compute the complement of the Boolean function  $F = A'B + AB' + A'C$  and implement the result using only NAND gates.
3. Find the complement of the Boolean function  $F = A \cdot (B + C) + A' \cdot (B \cdot C)$  using Boolean algebra and draw its corresponding logic circuit.
4. Derive the complement of  $F = AB + A'B'C$  using Boolean identities.
5. Using Boolean algebra, derive the complement of the function  $F = (A + B') \cdot (C + D') \cdot (A' + B)$ .

#### 5. Karnaugh Maps: 3-variable, 4-variable, 5-variable

1. Simplify the Boolean function  $F(A, B, C) = A'BC + AB'C + AB'C'$  using a 3-variable Karnaugh map.
2. Simplify the Boolean expression  $F(A, B, C, D) = AB + A'C + BD$  using a 4-variable Karnaugh map and draw the simplified circuit.
3. Use a 4-variable Karnaugh map to simplify the Boolean function  $F(A, B, C, D) = A'B'C + A'BC + AB'C'$  and show the steps for minimal expression.
4. Simplify the 5-variable Boolean function  $F(A, B, C, D, E) = AB'C + A'BC + C'D$  using a 5-variable Karnaugh map.
5. Solve for the minimal expression using a Karnaugh map for  $F(A, B, C, D) = A'B'C + A'BC + AB'C' + ABCD$ .

#### 6. Prime Implicants

1. Find the prime implicants for the Boolean function  $F(A, B, C, D) = AB'C' + A'BC + AB'C$ .
2. Derive the prime implicants for  $F(A, B, C, D) = A'B + C'D + A'BC$  using a Karnaugh map.
3. Determine the prime implicants for the Boolean expression  $F(A, B, C, D) = A'BC + AB'C + B'D$ .
4. Using a Karnaugh map, find the prime implicants for the Boolean function  $F(A, B, C, D, E) = A'B + C'D + AB'C$ .
5. Find the minimal SOP form using the prime implicants for the function  $F(A, B, C, D) = ABCD + A'BC$ .

#### 7. NAND and NOR

1. Implement the function  $F(A, B, C) = A \cdot B + A' \cdot B'$  using only NAND gates and derive its truth table.
2. Show how to implement the Boolean expression  $F(A, B) = A + B$  using only NOR gates and provide the simplified logic circuit.
3. Convert the Boolean expression  $F(A, B, C) = AB + A'C$  into an equivalent logic circuit using only NAND gates.
4. Implement the following Boolean function  $F(A, B, C) = A \cdot (B + C) + A' \cdot B$  using only NOR gates.
5. Prove that NAND gates alone can be used to realize all the basic logic gates (AND, OR, NOT), and show the corresponding circuits.

## 8. Don't-Care Conditions

1. Simplify the Boolean function  $F(A, B, C) = AB + A'C$  using a Karnaugh map with the condition that  $F = 1$  when  $A = 0$  and  $B = 1$ .
2. Simplify  $F(A, B, C, D) = A'B + C'D$  using the Karnaugh map, where  $D = 1$  is a don't-care condition.
3. Minimize the Boolean function  $F(A, B, C, D) = AB + A'C + BD$  with the don't-care condition  $C = 1$ .
4. Simplify the expression  $F(A, B, C) = A'B + AC$  with a don't-care condition for  $B = 0$ .
5. Simplify the Boolean function  $F(A, B, C, D) = ABCD + A'B'C'$  considering the don't-care condition where  $C = 0$ .

## Questions from references

The following questions are referenced from the book *Digital Design with an Introduction to the Verilog HDL, Fifth Edition* by M. Morris Mano and Michael D. Ciletti. The questions could help in deeper understanding and exploration.

### Chapter 1

☐ 1.5      ☐ 1.6      ☐ 1.9

### Chapter 2

☐ 2.4      ☐ 2.8      ☐ 2.9      ☐ 2.10      ☐ 2.14   ☐ 2.18      ☐ 2.19      ☐ 2.20  
☐ 2.22      ☐ 2.30      ☐ 2.31

### Chapter 3

☐ 3.4      ☐ 3.7      ☐ 3.9      ☐ 3.10      ☐ 3.17   ☐ 3.23      ☐ 3.28      ☐ 3.29

### Chapter 4

☐ 4.5      ☐ 4.8      ☐ 4.9      ☐ 4.11      ☐ 4.12   ☐ 4.28      ☐ 4.29      ☐ 4.33

### Chapter 5

☐ 5.2      ☐ 5.3      ☐ 5.6      ☐ 5.9      ☐ 5.10   ☐ 5.11